 


Lecture 7 : Logical Effort

CSCI 5330 Digital CMOS VLSI Design


Instructor: Saraju P. Mohanty, Ph. D.

NOTE: The figures, text etc included in slides are borrowed from various books, websites, authors pages, and other sources for academic purpose only. The instructor does not claim any originality.




Outline

 - Delay in a Logic Gate
- Multistage Logic Networks
- Choosing the Best Number of Stages
- Limitations of Logical Effort




Introduction

- Chip designers face a bewildering array of choices
 - What is the best circuit topology for a function?
 - How many stages of logic give least delay?
 - How wide should the transistors be?
- Logical effort is a method to make these decisions
 - Uses a simple model of delay
 - Allows back-of-the-envelope calculations
 - Helps make rapid comparisons between alternatives
 - Emphasizes remarkable symmetries

 

Delay in a Logic Gate

 - Example : Estimate the frequency of an N-stage ring oscillator



Logical Effort: $g = 1$


Electrical Effort: $h = 1$

Parasitic Delay: $p = 1$

Stage Delay: $d = 2$


Frequency: $f_{osc} = 1/(2*N*d) = 1/4N$

 31 stage ring oscillator in
0.6 μm process has
frequency of ~ 200 MHz



Delay in a Logic Gate

 - Estimate the delay of a fanout-of-4 (FO4) inverter



Logical Effort: $g = 1$

Electrical Effort: $h = 4$

Parasitic Delay: $p = 1$


Stage Delay: $d = 5$

The FO4 delay is about

200 ps in 0.6 μm process

60 ps in a 180 nm process

$f/3$ ns in an f μm process

 

Multistage Logic Networks

- Logical effort generalizes to multistage networks
- *Path Logical Effort*


$$G = \prod g_i$$


- *Path Electrical Effort*

$$H = \frac{C_{\text{out-path}}}{C_{\text{in-path}}}$$

- *Path Effort*

$$F = \prod f_i = \prod g_i h_i$$

 

 

Multistage Logic Networks

- Logical effort generalizes to multistage networks
- *Path Logical Effort*

$$G = \prod g_i$$


- *Path Electrical Effort*

$$H = \frac{C_{out-path}}{C_{in-path}}$$

- *Path Effort*

$$F = \prod f_i = \prod g_i h_i$$

- Can we write $F = GH$?

 

Multistage Logic Networks : Paths that Branch

- No! Consider paths that branch:

$$G = 1$$


$$H = 90 / 5 = 18$$


$$GH = 18$$

$$h_1 = (15 + 15) / 5 = 6$$

$$h_2 = 90 / 15 = 6$$

$$F = g_1 g_2 h_1 h_2 = 36 = 2GH$$

 

 

Multistage Logic Networks : Branching Effort

- Introduce *branching effort*
 - Accounts for branching between stages in path


$$b = \frac{C_{\text{on path}} + C_{\text{off path}}}{C_{\text{on path}}}$$

$$B = \prod b_i$$

Note:

$$\prod h_i = BH$$

 - Now we compute the path effort
 - $F = GBH$



Multistage Logic Networks : Multistage Delays

- Path Effort Delay


$$D_F = \sum f_i$$

- Path Parasitic Delay

$$P = \sum p_i$$

- Path Delay

$$D = \sum d_i = D_F + P$$

 

Multistage Logic Networks : Designing Fast Circuits

$$D = \sum d_i = D_F + P$$


- Delay is smallest when each stage bears same effort

$$\hat{f} = g_i h_i = F^{\frac{1}{N}}$$

- Thus minimum delay of N stage path is

$$D = NF^{\frac{1}{N}} + P$$

 - This is a **key** result of logical effort
 - Find fastest possible delay
 - Doesn't require calculating gate sizes




Multistage Logic Networks : Gate Sizes

- How wide should the gates be for least delay?


$$\hat{f} = gh = g \frac{C_{out}}{C_{in}}$$
$$\Rightarrow C_{in_i} = \frac{g_i C_{out_i}}{\hat{f}}$$

 
- Working backward, apply capacitance transformation to find input capacitance of each gate given load it drives.
- Check work by verifying input cap spec is met.



Multistage Logic Networks : 3-stage path

 
- Example: Select gate sizes x and y for least delay from A to B



 

Multistage Logic Networks :

3-stage path Example

 

Logical Effort $G = (4/3) * (5/3) * (5/3) = 100/27$

Electrical Effort $H = 45/8$


Branching Effort $B = 3 * 2 = 6$

Path Effort $F = GBH = 125$

Best Stage Effort $\hat{f} = \sqrt[3]{F} = 5$

Parasitic Delay $P = 2 + 3 + 2 = 7$

 Delay $D = 3 * 5 + 7 = 22 = 4.4 \text{ FO4}$




Multistage Logic Networks :


3-stage path Example

- Work backward for sizes

$$y = 45 * (5/3) / 5 = 15$$

$$x = (15 * 2) * (5/3) / 5 = 10$$

 


 


Choosing Best Number of Stages

- How many stages should a path use?
 - Minimizing number of stages is not always fastest
- Example: drive 64-bit datapath with unit inverter

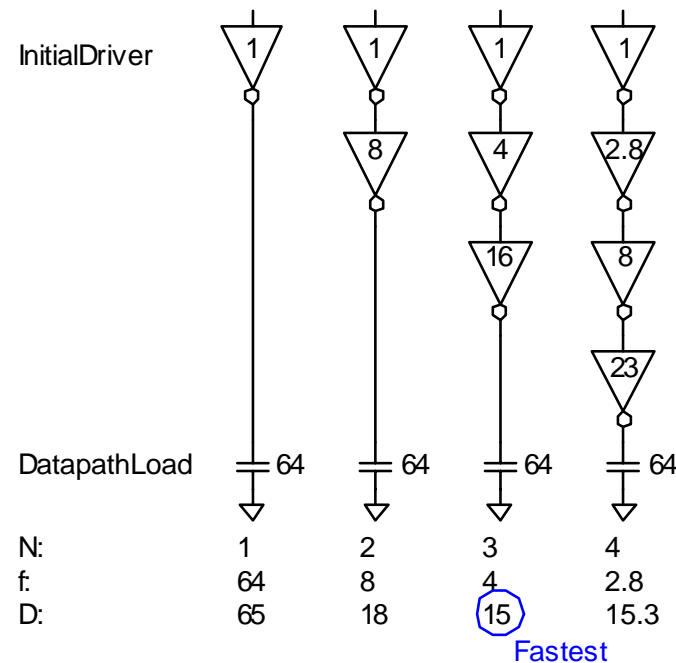
$$D = NF^{1/N} + P$$
$$= N(64)^{1/N} + N$$



 

Choosing Best Number of Stages

- Consider adding inverters to end of path
 - How many give least delay?
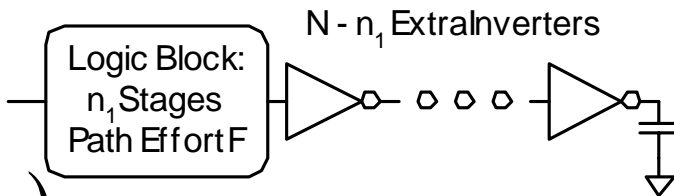
$$D = NF^{\frac{1}{N}} + \sum_{i=1}^{n_1} p_i + (N - n_1) p_{inv}$$


 
The diagram shows a logic block labeled 'Logic Block: n₁ Stages Path Effort F' connected to a series of inverters. The first inverter is connected to the logic block, and the subsequent inverters are connected in a chain. The chain ends with an inverter connected to ground. The text 'N - n₁ Extra Inverters' is written above the chain of inverters.

$$\frac{\partial D}{\partial N} = -F^{\frac{1}{N}} \ln F^{\frac{1}{N}} + F^{\frac{1}{N}} + p_{inv} = 0$$

- Define best stage effort


$$\rho = F^{\frac{1}{N}}$$

$$p_{inv} + \rho(1 - \ln \rho) = 0$$




Choosing Best Number of Stages : Best Stage Effort

 - $p_{inv} + \rho(1 - \ln \rho) = 0$ has no closed-form solution
- Neglecting parasitics ($p_{inv} = 0$), we find $\rho = 2.718$ (e)
- For $p_{inv} = 1$, solve numerically for $\rho = 3.59$




Choosing Best Number of Stages : Sensitivity Analysis

 - How sensitive is delay to using exactly the best number of stages?



 
- $2.4 < \rho < 6$ gives delay within 15% of optimal
 - We can be sloppy!
 - I like $\rho = 4$



Spreadsheet Comparison


- Compare many alternatives with a spreadsheet

Design	N	G	P	D
NAND4-INV	2	2	5	29.8
NAND2-NOR2	2	20/9	4	30.1
INV-NAND4-INV	3	2	6	22.1
NAND4-INV-INV-INV	4	2	7	21.1
NAND2-NOR2-INV-INV	4	20/9	6	20.5
NAND2-INV-NAND2-INV	4	16/9	6	19.7
INV-NAND2-INV-NAND2-INV	5	16/9	7	20.4
NAND2-INV-NAND2-INV-INV-INV	6	16/9	8	21.6

 

Review of Definitions

Term	Stage	Path
number of stages	1	N
logical effort	g	$G = \prod g_i$
electrical effort	$h = \frac{C_{out}}{C_{in}}$	$H = \frac{C_{out-path}}{C_{in-path}}$
branching effort	$b = \frac{C_{on-path} + C_{off-path}}{C_{on-path}}$	$B = \prod b_i$
effort	$f = gh$	$F = GBH$
effort delay	f	$D_F = \sum f_i$
parasitic delay	p	$P = \sum p_i$
delay	$d = f + p$	$D = \sum d_i = D_F + P$

 

Method of Logical Effort

1) Compute path effort

$$F = GBH$$

2) Estimate best number of stages

$$N = \log_4 F$$

3) Sketch path with N stages

4) Estimate least delay


$$D = NF^{\frac{1}{N}} + P$$

5) Determine best stage effort

$$\hat{f} = F^{\frac{1}{N}}$$

 6) Find gate sizes

$$C_{in_i} = \frac{g_i C_{out_i}}{\hat{f}}$$



Limitations of Logical Effort

- Chicken and egg problem
 - Need path to compute G
 - But don't know number of stages without G
- Simplistic delay model
 - Neglects input rise time effects
- Interconnect
 - Iteration required in designs with wire
- Maximum speed only
 - Not minimum area/power for constrained delay