

CSCE 5730: Digital CMOS VLSI Design

Assignment # 3, Total Marks = $4 \times 25 = 100$.

Assigned Date: 2nd Apr 2008 (Wed), Due Date: 9th Apr 2008 (Wed)

Instructor: Dr. Saraju P. Mohanty

1. Design a 4:1 mux using transmission gates and simulate it using LTspice. (20-points)
2. Design a D flip-flop using transmission gates and simulate using LTspice. (20-points)
3. Simulate the above flip-flop for non-overlapping clocks using LTspice. (20-points)
4. Using NMOS models produce its current-voltage characteristics. Use a spreadsheet or MATLAB for the purpose. Assume the parameters from any text book. (20-points)
5. Read literature and discuss alpha-power law model for transistors. (20-points)